
SHIFT REGISTER

Create a circuit that will shift a 16-bit binary number. On a falling edge:

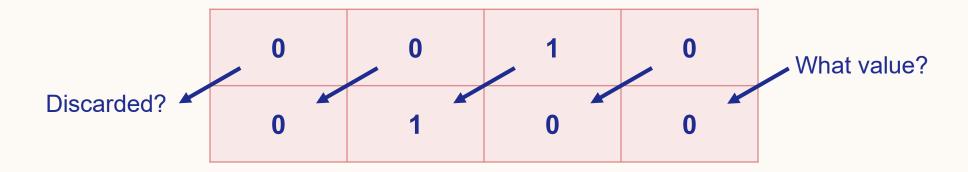- If load is high, should load the value from in
- If *shift* is high, should load the previous value "shifted" by one place to the left



You may assume *load* and *shift* are not high at the same time...